



Please write clearly in block capitals.

Centre number

Candidate number

Surname _____

Forename(s) _____

Candidate signature _____

I declare this is my own work.

Level 3 Certificate/Extended Certificate

APPLIED SCIENCE

Unit 1 Key Concepts in Science
Section C – Physics

Tuesday 17 January 2023

Morning

Time allowed: 1 hour 30 minutes.

Materials

For this paper you must have:

- a calculator
- the Formulae Sheet (enclosed).

You are advised to spend approximately 30 minutes on this section.

Instructions

- Use black ink or black ball-point pen.
- Fill in the boxes at the top of this page.
- Answer **all** questions in each section.
- You must answer the questions in the spaces provided. Do not write outside the box around each page or on blank pages.
- If you need extra space for your answer(s), use the lined pages at the end of this book. Write the question number against your answer(s).
- Do all rough work in this book. Cross through any work you do not want to be marked.

For Examiner's Use	
Question	Mark
1	
2	
TOTAL	

Information

- You will be provided with a copy of the Formulae Sheet.
- There are three sections in this paper:
Section A – Biology **Section B** – Chemistry **Section C** – Physics.
- The marks for questions are shown in brackets.
- The maximum mark for this paper is 60 and the maximum mark for this section is 20.

Advice

Read each question carefully.



J A N 2 3 A S C 1 P O 1

IB/M/Jan23/E5

ASC1/P

Section C – Physics

Answer **all** the questions in this section.

0 1

A student investigated the voltage and current for a lamp.

Figure 1 shows a circuit diagram for the student's circuit.

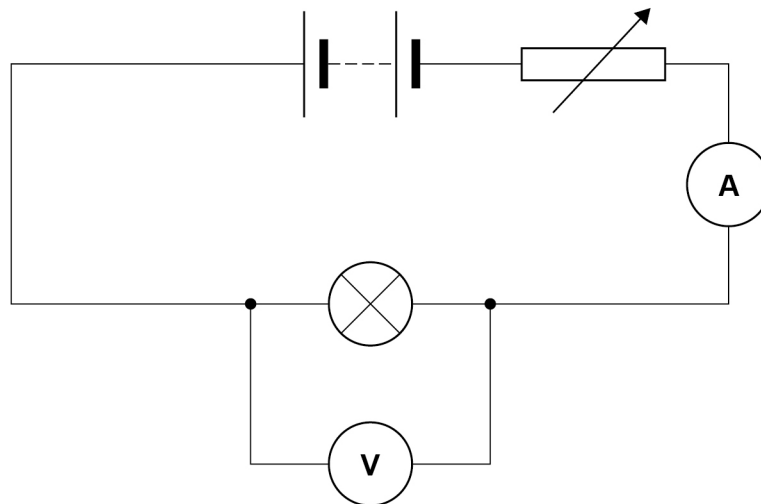
Figure 1

Table 1 shows the results.

Table 1

Voltage / V	0.00	2.00	4.00	6.00	8.00	10.00	12.00
Current / A	0.00	0.80	1.20	1.52	1.72	1.88	2.00

0 1 . 1

Name the component in **Figure 1** that is used to change the voltage across the lamp.

[1 mark]

0 1 . 2


Plot a graph of the results shown in **Table 1** on **Figure 2**.

The first three points have been plotted for you.

Draw a line of best fit.

[2 marks]

Figure 2

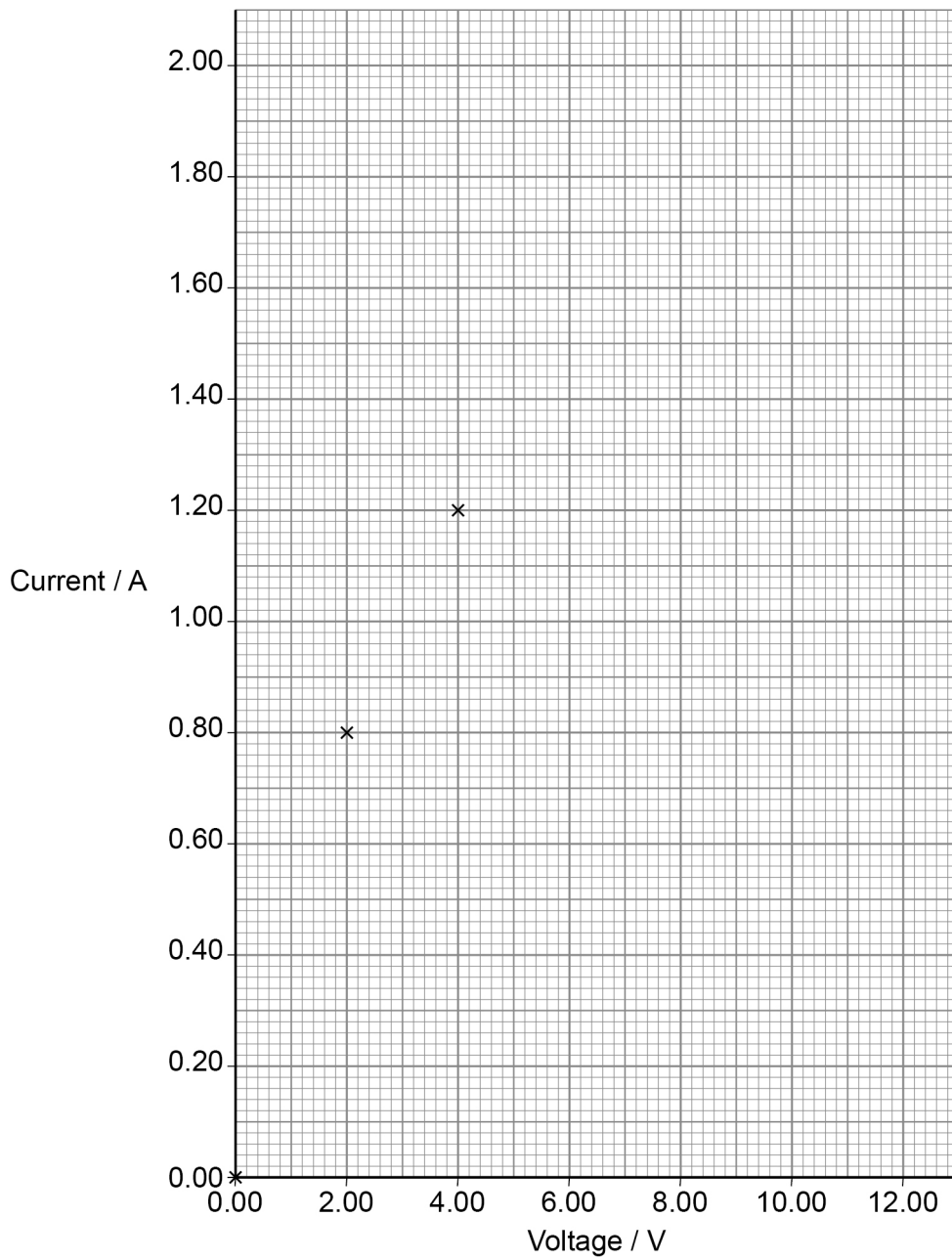

0 1 . 3 Calculate the resistance of the lamp when the voltage is 1.00 V.

Give the unit.

Use the Formulae Sheet and data from **Figure 2**.

[3 marks]

Resistance of the lamp = _____ Unit _____

Question 1 continues on the next page

Turn over ►



0 1 . 4 The resistance of the lamp increases as the voltage increases.

How does your line of best fit on **Figure 2** show this?

[1 mark]

0 1 . 5 Explain why the resistance of the lamp increases as the voltage increases.

You should refer to electrons in your answer.

[3 marks]

Table 1 is repeated below.

Table 1

Voltage / V	0.00	2.00	4.00	6.00	8.00	10.00	12.00
Current / A	0.00	0.80	1.20	1.52	1.72	1.88	2.00

0 1 . 6 Calculate the maximum power of the lamp in this investigation.

Use the Formulae Sheet and data from **Table 1**.

[1 mark]

Maximum power of the lamp = _____ W

11



0 2

A car is driven in a race.

The car accelerates from rest with a **constant** acceleration of 10.2 m s^{-2} for 1.7 seconds.

0 2 . 1

Calculate the speed of the car at 1.7 seconds.

Use the Formulae Sheet.

[1 mark]

Speed of car at 1.7 seconds = _____ m s^{-1}

0 2 . 2

The mass of the car is 1500 kg.

Calculate the driving force of the car's engine.

Give the unit.

Use the Formulae Sheet.

[2 marks]

Driving force of the engine = _____ Unit _____





Question 2 continues on the next page

Turn over ►

0 2 . 3

Which of the following graphs **A**, **B**, **C** or **D** shows how the displacement of the car changes as it accelerates during the first 1.7 seconds of the race?

[1 mark]

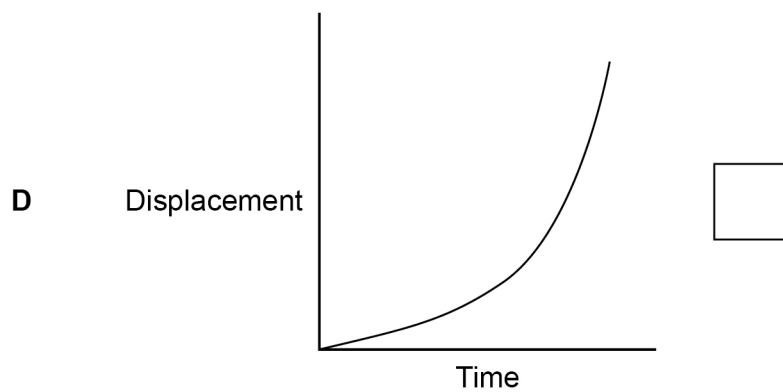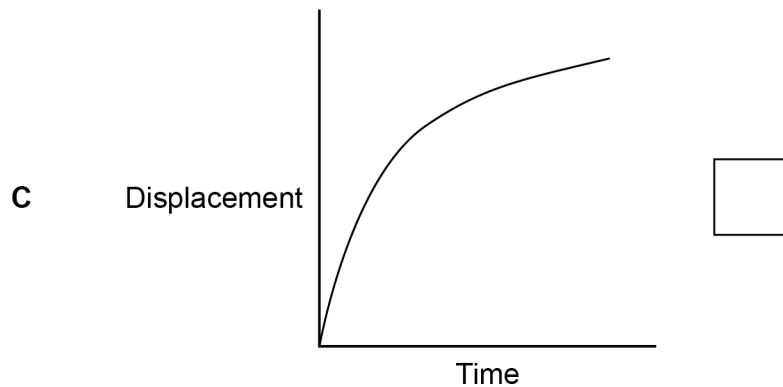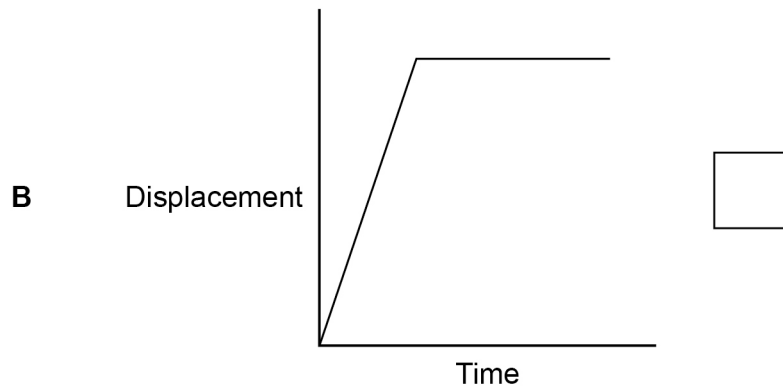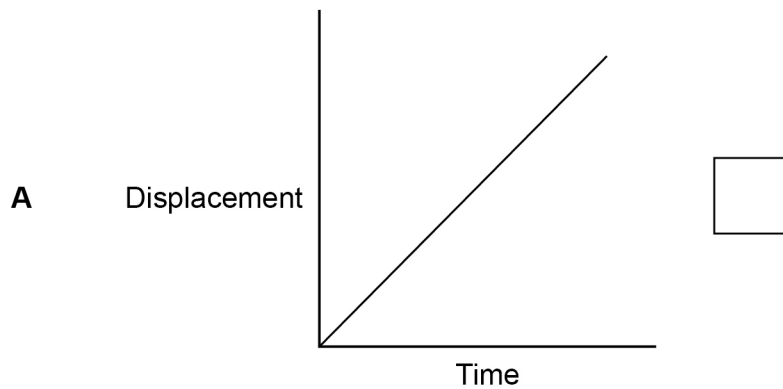Tick (✓) **one** box.

0 2 . 4 The driving force of the car's engine is the same throughout the race.

However, after 1.7 seconds the acceleration of the car is **not** constant.

Explain why the acceleration of the racing car is **not** constant after 1.7 seconds.

In your answer, you should refer to the forces involved.

[3 marks]

0 2 . 5 At the end of the race the driver applies the brakes to stop the car.

Describe the energy transfers when the brakes are applied

[2 marks]

9

END OF QUESTIONS



There are no questions printed on this page

*Do not write
outside the
box*

**DO NOT WRITE ON THIS PAGE
ANSWER IN THE SPACES PROVIDED**



There are no questions printed on this page

*Do not write
outside the
box*

**DO NOT WRITE ON THIS PAGE
ANSWER IN THE SPACES PROVIDED**

Copyright information

For confidentiality purposes, all acknowledgements of third-party copyright material are published in a separate booklet. This booklet is published after each live examination series and is available for free download from www.aqa.org.uk.

Permission to reproduce all copyright material has been applied for. In some cases, efforts to contact copyright-holders may have been unsuccessful and AQA will be happy to rectify any omissions of acknowledgements. If you have any queries please contact the Copyright Team.

Copyright © 2023 AQA and its licensors. All rights reserved.



1 2



2 3 1 A A S C 1 / P

IB/M/Jan23/ASC1/P